

A vertical bar on the left side of the slide, composed of several colored segments: a small grey rectangle at the top, followed by a white section, then a yellow segment, and a long pink segment at the bottom.

# LAB 2

HOME ASSIGNMENT




# Home assignment Goal

FPGA-based Image processing:

1. Send/receive images via UART
2. Color-to-Gray (C2G) conversion
3. Save Gray image in BRAM
4. Check correct image dimension
5. Edge detection via image convolution




# Block Diagram

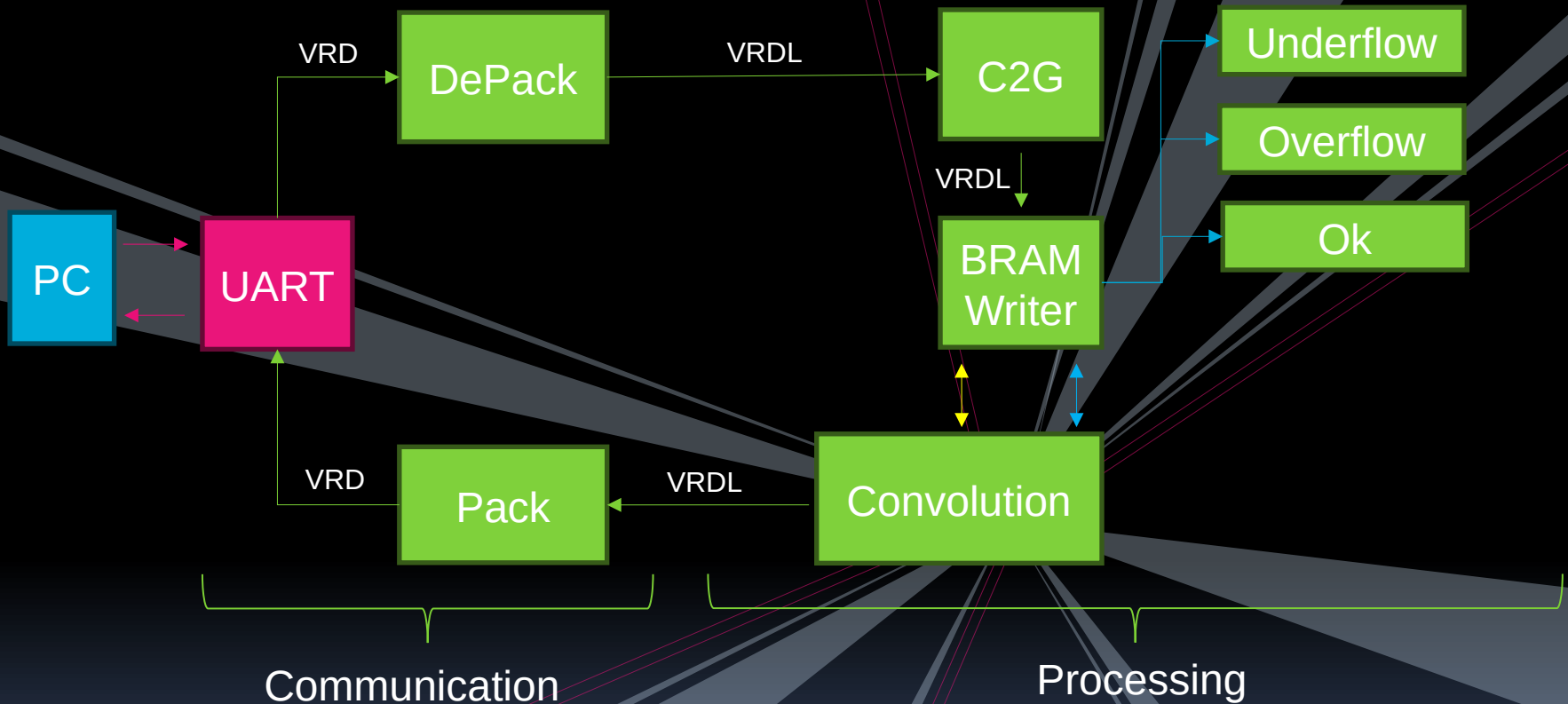



# Communication loopback (I)


NB: use the smallest possible buffering!

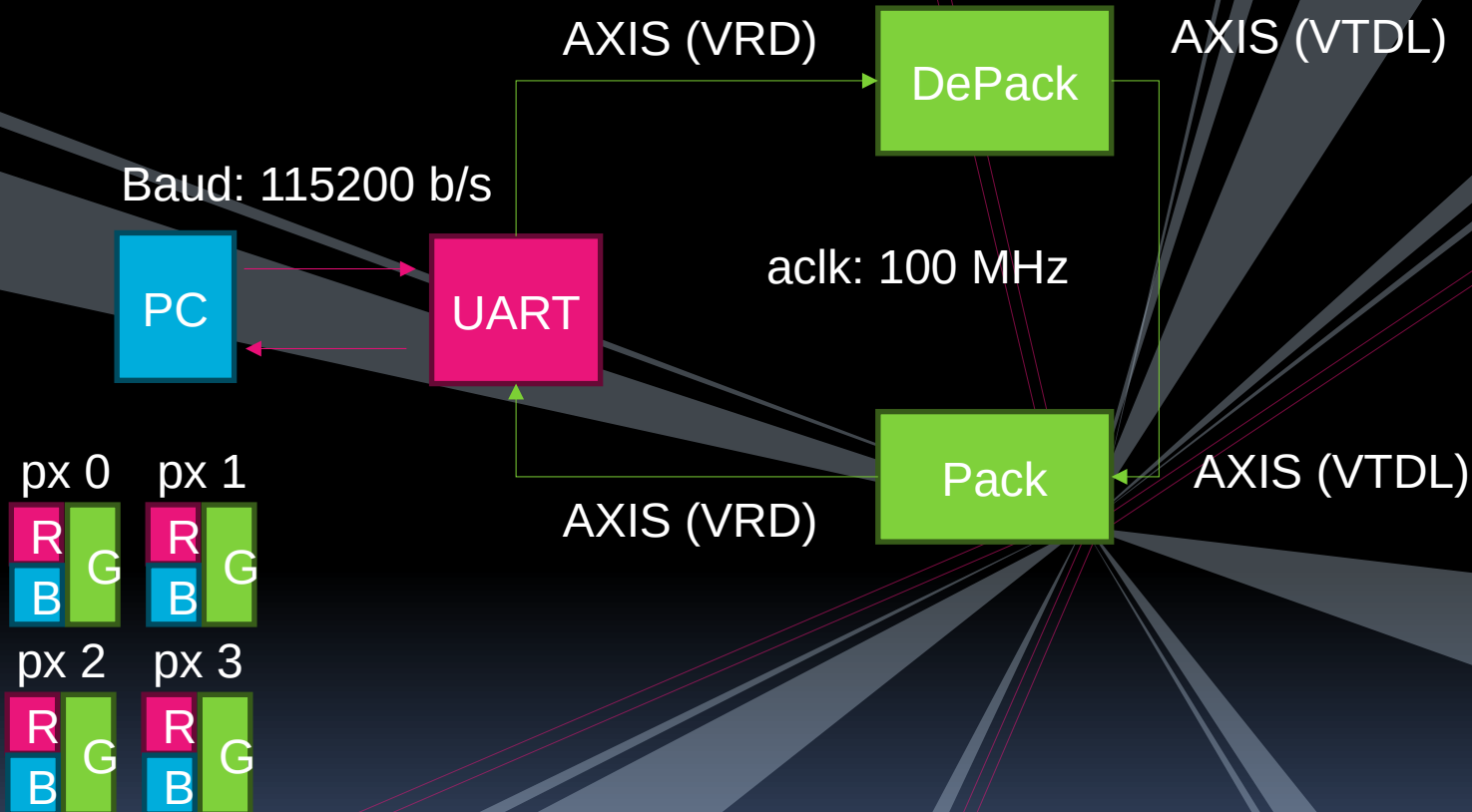



# Communication loopback (II)

NB: use the smallest possible buffering!

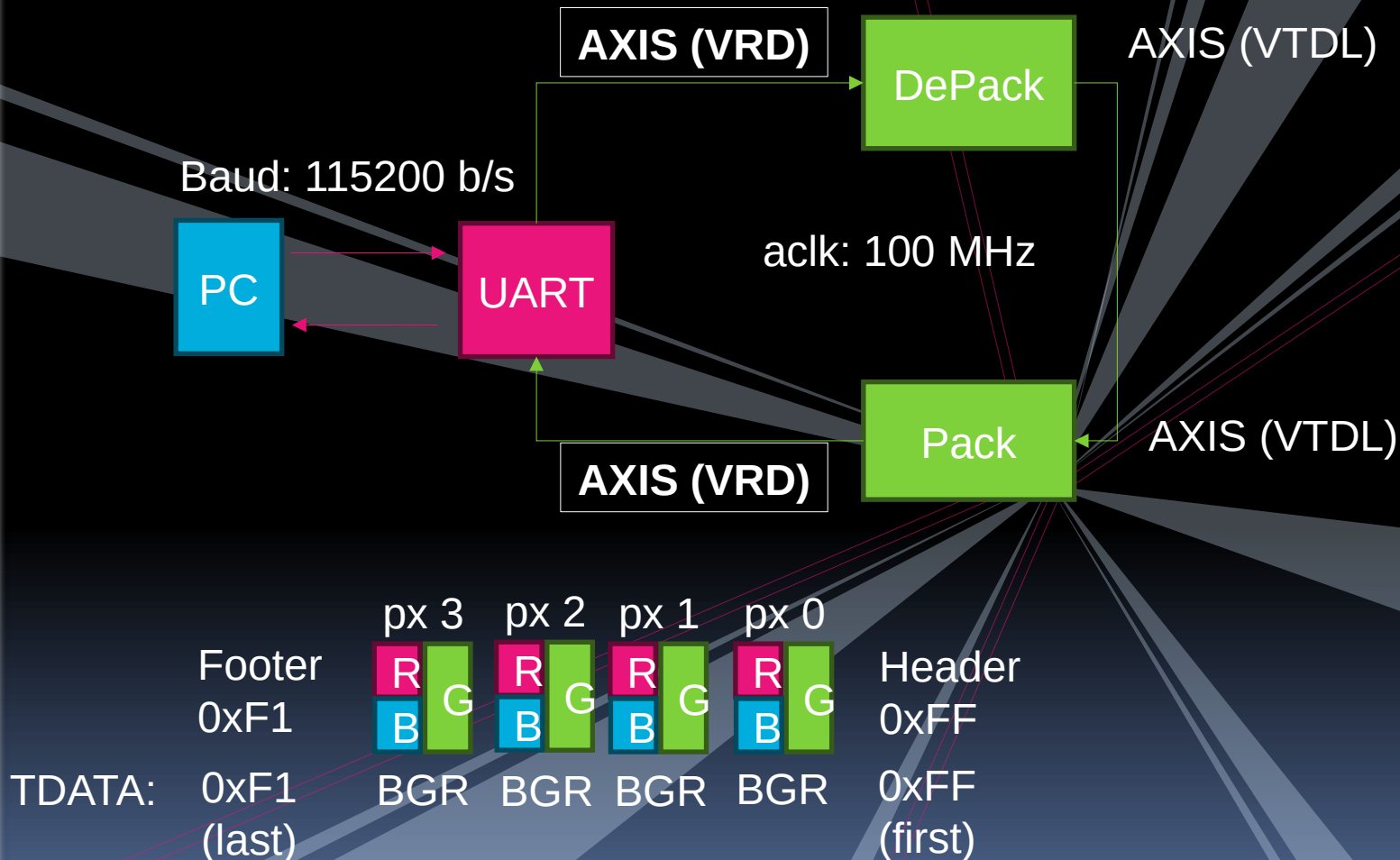


TDATA is 8 bit, RGB are in range 0-to-127



# Communication loopback (III)

NB: use the smallest possible buffering!

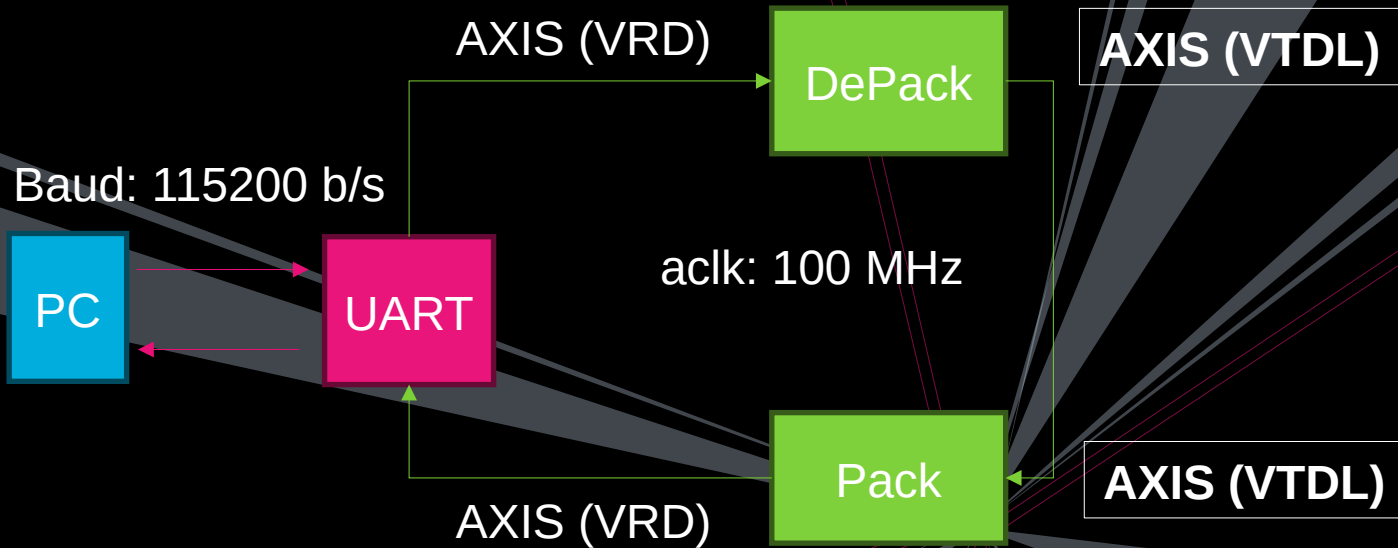


	px 3	px 2	px 1	px 0
	 	 	 	 
TDATA:	BGR	BGR	BGR	BGR
TLAST:	1 0 0	0 0 0	0 0 0	0 0 0

TDATA is 8 bit, **RGB** are in range 0-to-127



# Color-to-Gray (I)

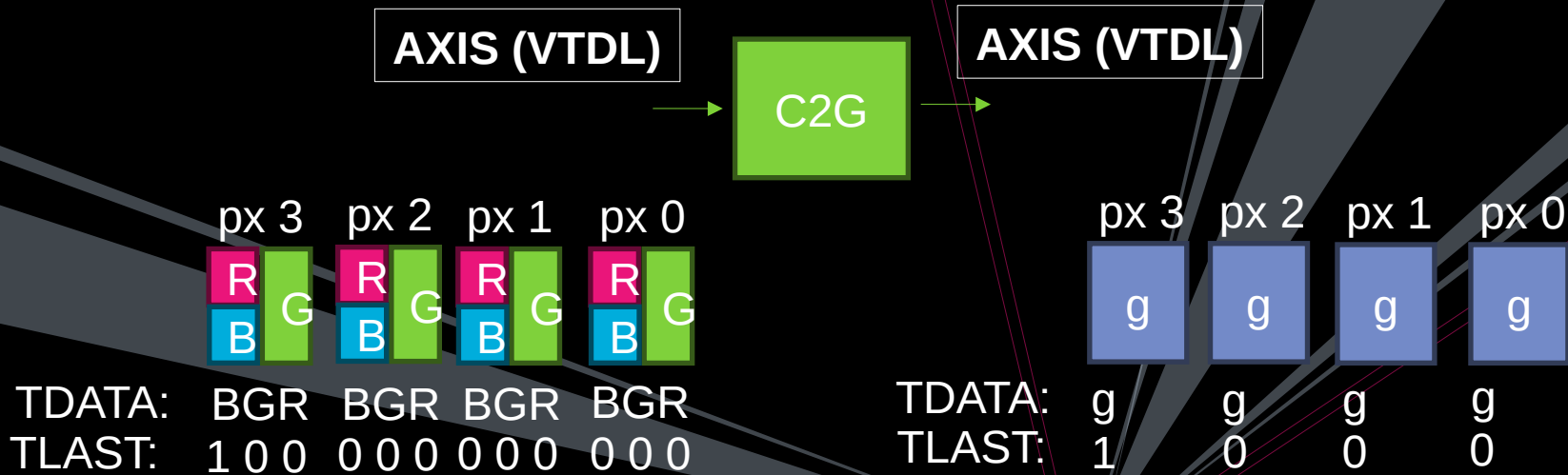

$$g = (R + G + B)/3$$


E.g.:

- $5 + 5 + 5 \Rightarrow 5$
- $127 + 127 + 127 \Rightarrow 127$
- $1 + 2 + 1 \Rightarrow 1 \text{ or } 2 (*)$

(\*): implement the “/3” as a submodule of C2G and work with integer/unsigned and approximation; explain your decisions.

NB: use the smallest possible buffering!

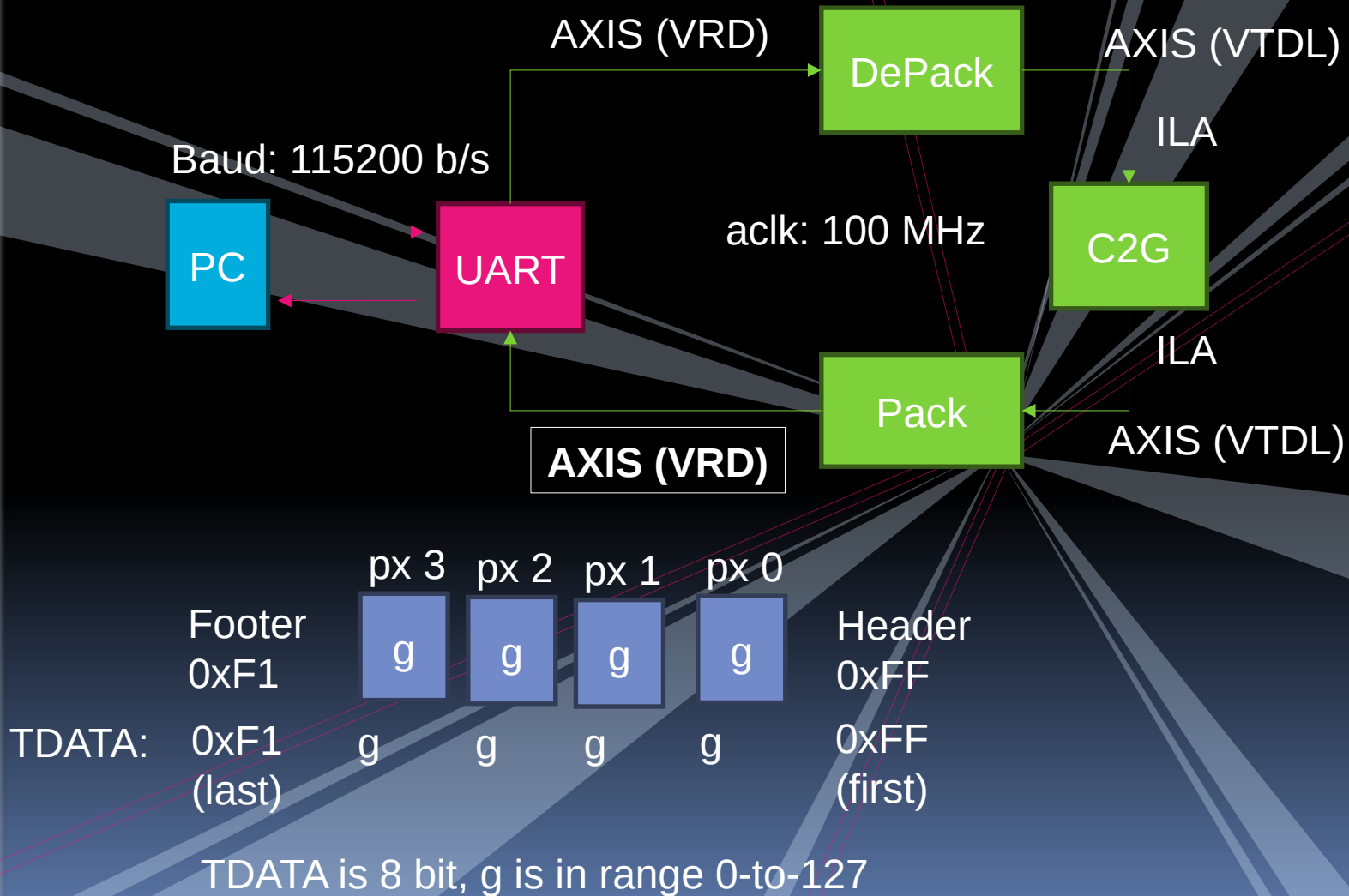
TDATA is 8 bit, RGB and g are in range 0-to-127







# BRAM Writer (I)

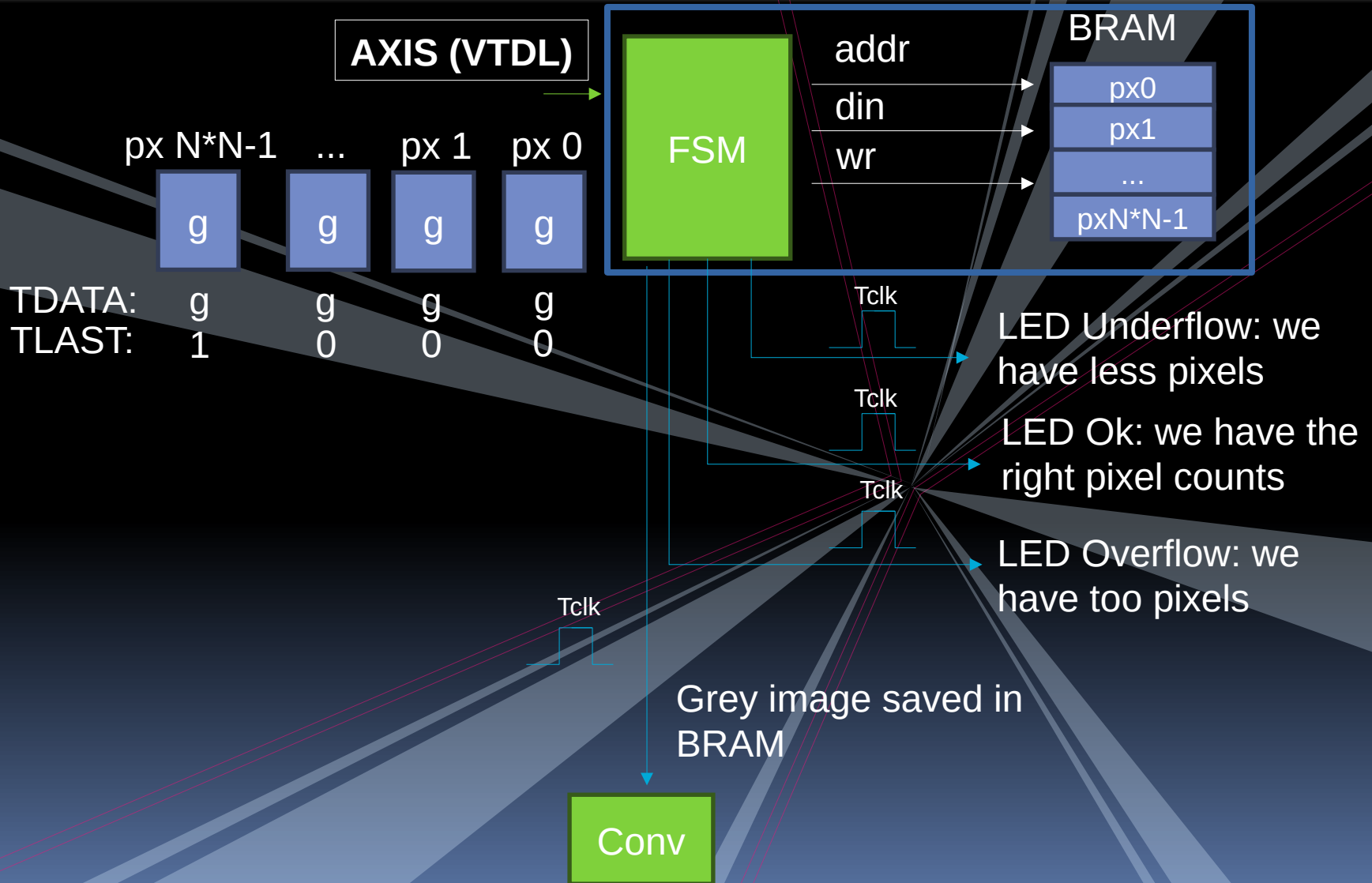



# BRAM Writer (II)

AXIS (VTDL)  
Do not read AXIS!

FSM

BRAM

px0

px1

...

pxN\*N-1

dout

Tclk

Start Convolution

addr

Conv






# BRAM Writer (III)

Optionally write yourself a VHDL tesbench to simulate the BRAM writer and/or use an ILA.




# Convolution (I)



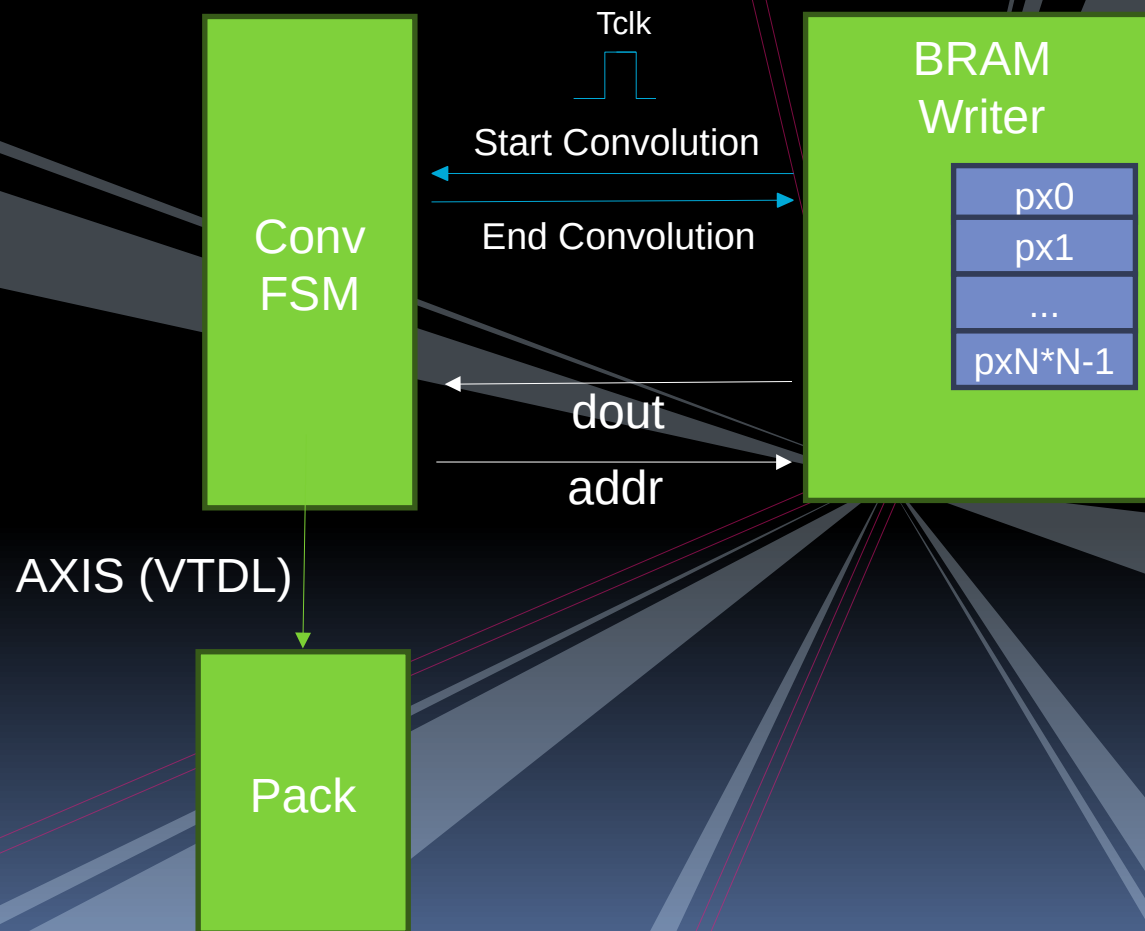




# Convolution (II)

 


Sums of 9  
Cell-by-Cell  
products

   



# Convolution (III)

 

Use zero if the convolution matrix has cells without pixels

Cells of convolution matrix are *signed(7 downto 0)*

Pixels of grey image are *unsigned(7 downto 0)*

Attention:

- The 9 Cell-to-cell products are signed
- The sum of the 9 cell-to-cell product is signed
- Resize the result of the convolution as *unsigned(7 downto 0)* as follow:
  - If  $\text{conv} < 0 \Rightarrow$  is 0
  - If  $\text{conv} > 128 \Rightarrow$  is 127




# Convolution (IV)

TestBench is provided



# LED Blinking

 

LED Blinking

4 blinking: 1 sec on and 1 sec off.





# Delivery

1. Communication loopback (UART + Pack + Depack)
2. Replace the encrypted modules with yours in the final project
3. If you write TestBench please provide it to us.
4. Default parameters are specified in the project/VHDL templates
5. Compile the final project with default parameters
6. Archive the full projects (from Vivado) for delivery



# File List

1. DESD-LAB2-ENCRYPTED.xpr.zip, encrypted project
2. design\_1\_wrapper.bit/ltx bitstream and waveform ILA
3. DESD-LAB2-Template.srcs.zip, VHDL templates
4. test.py, send image via UART using python
5. LAB2-Test, test.py compiled for Linux OS
6. LAB2-Test.exe, test.py compiled for Windows OS
7. test1.png and test2.png images

**WARNING:** When execute the provided programs ensure that test1.png and test2.png images are in the same folder of the executable.



# Correction Rules

- Led Blinking, 1 pt
- Depack, 2 pt
- Pack, 2 pt
- Color-to-Gray, 2 pt
- BRAM writer, 2 pt
- Convolution, 2 pt